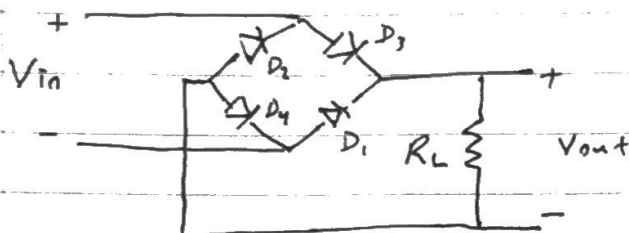


Quiz 2.




$$V_{D_{on}} = 750 \text{ mV}$$

$$V_{in} = V_p \cos 2\pi f t$$


$$V_p = 6 \text{ V}$$

$$f = 60 \text{ Hz}$$

a) Input/output characteristics

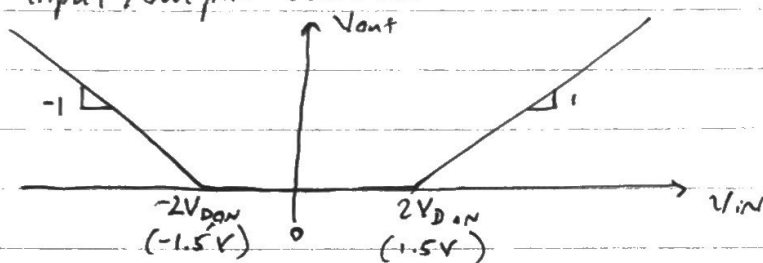

V_{out} vs. time

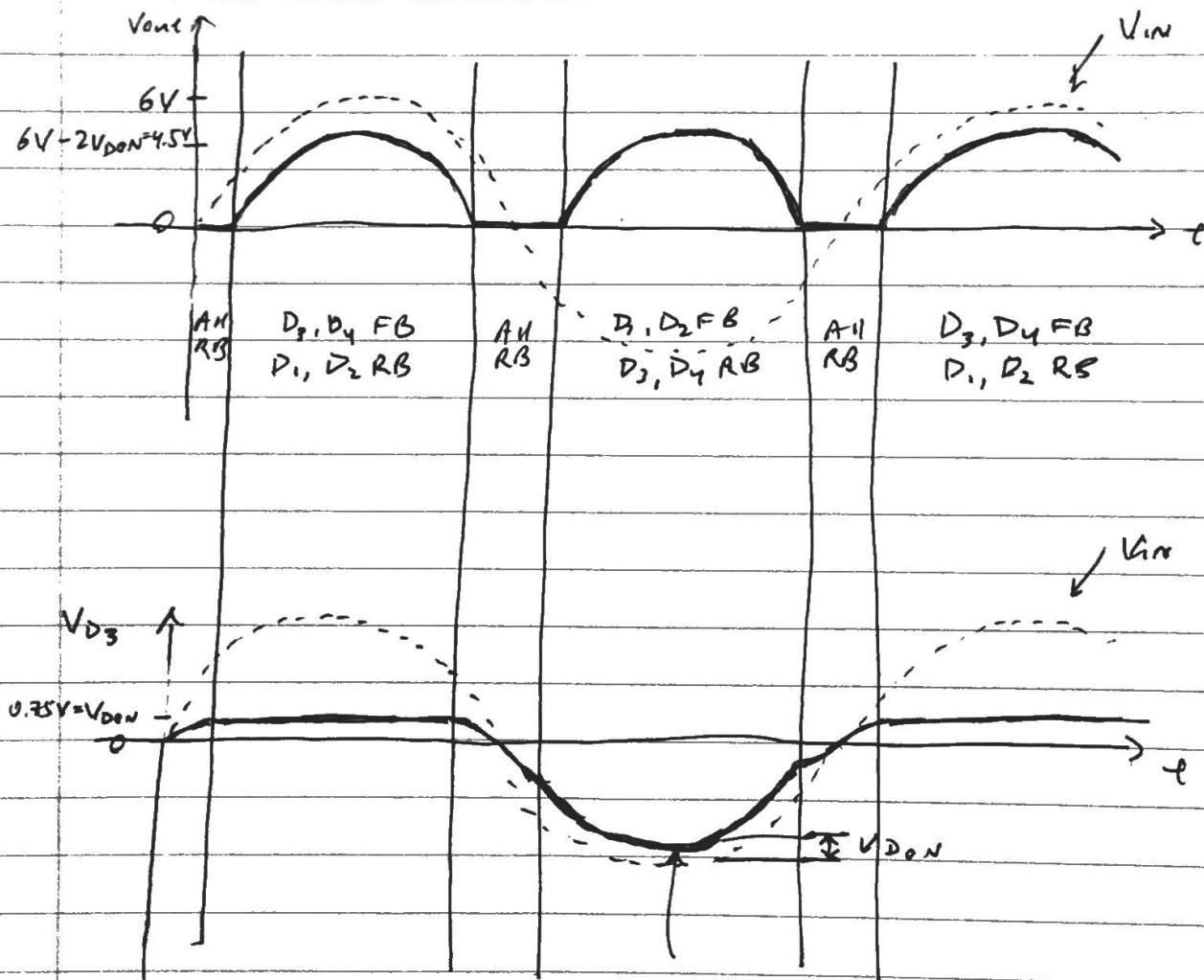

$$PIV = -6 \text{ V} + V_{D_{on}} = -5.25 \text{ V}$$

Quiz 2.

- b) $V_{rmax} = 0.4V$, $R_L = 50\Omega$, add smoothing cap. in parallel to load.



$$V_r = \frac{I_L}{Cf}$$

$$f = 2 \times 60Hz = 120Hz$$

full wave rectifier doubles ripple freq.

$$I_L = \frac{V_L}{R_L} = \frac{V_p - 2V_{D,on}}{R_L} = \frac{4.5V}{50\Omega} = 90mA$$
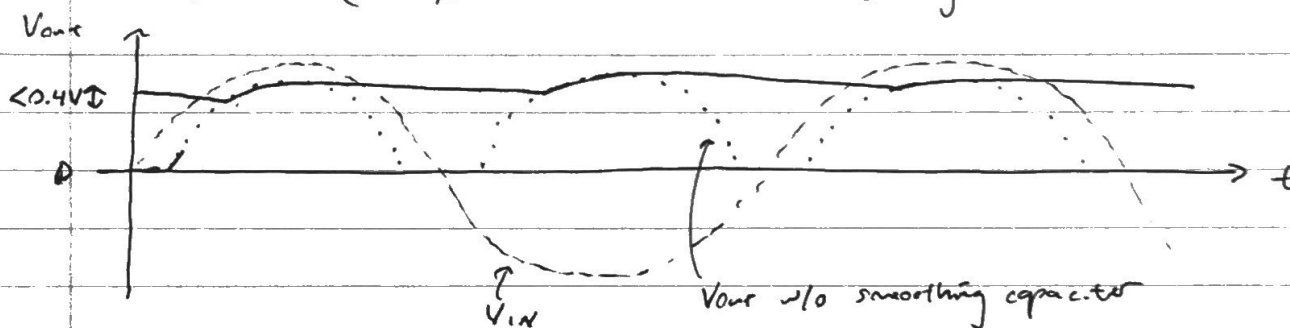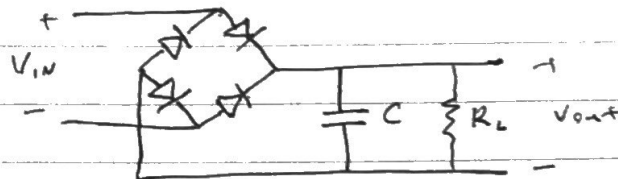
$$C = \frac{I_L}{V_r f} = \frac{90mA}{(0.4V)(120Hz)} = 1.875mF \text{ (or greater)}$$



- c) $R_1 = 100\Omega$, D_1 : $V_{D,on} = 800mV$, D_2 : $V_{D_2} = 3.2V$, $r_{d2} = 5\Omega$.
Calculate line & load regulation.


Line regulation:

assume small signal model

(center of ripple) $I_D = \frac{4.3V - 4V}{100\Omega} = 3mA$

$$r_d = \frac{V_T}{I_D} = \frac{0.026V}{0.003A} = 8.67\Omega$$


approximate w/ small signal model:

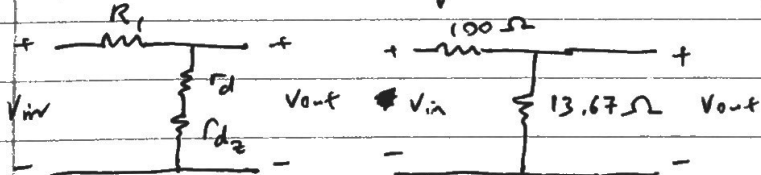

$$V_{out} = \frac{13.67\Omega}{(13.67 + 100)\Omega} V_{in}$$

$$\Delta V_{out} = \frac{13.67}{113.67} \Delta V_{in}$$
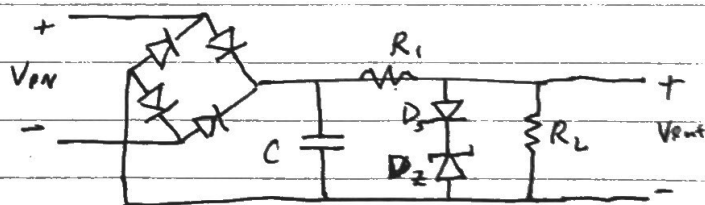
$$\text{line voltage regulation} = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{13.67}{113.67} \times 100\% = 12.03\%$$




Load regulation: (assume 50Ω load)

$$I_{R_L} = -\Delta I_{D_{grounded}} = \frac{V_{regulated}}{R_L} = \frac{4V}{50\Omega} = 80mA$$

$$\Delta V_{loaded} = (\Delta I_{D_{loaded}})(r_d) = (-80mA)(13.67\Omega) = -1.09V$$

$$\text{load regulation} = \frac{\Delta V_{loaded}}{V_{regulated}} = \frac{-1.09V}{4V} = -27.3\%$$




Quiz 2.

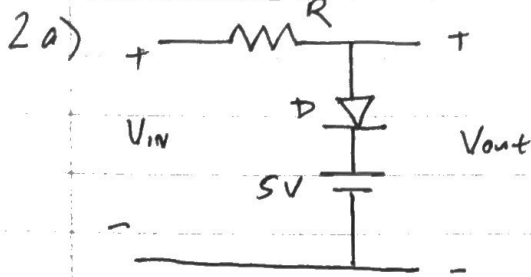

$$V_{D,on} = 0.7V$$

$$V_{in} = V_p \cos \omega t, \quad V_p = 6V$$


input/output characteristic:

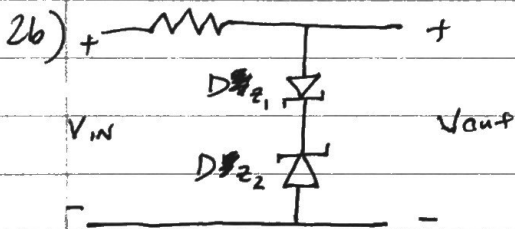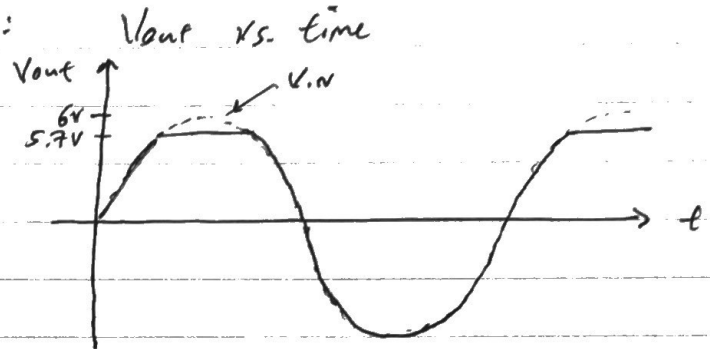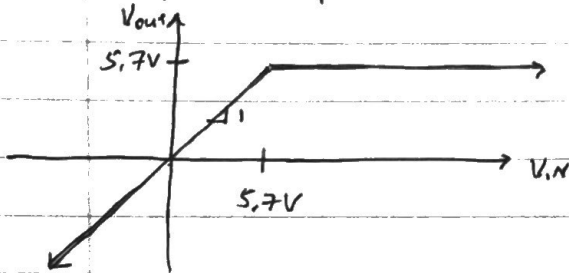



$$V_z = 2V$$

$$V_{in} = (\text{same as above})$$

input/output characteristic:

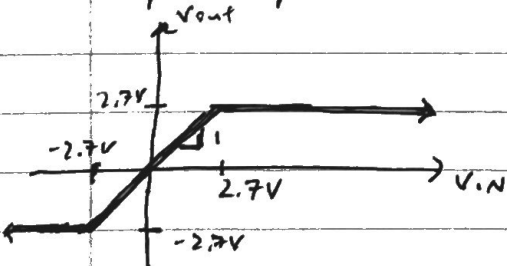


V_out vs. time:

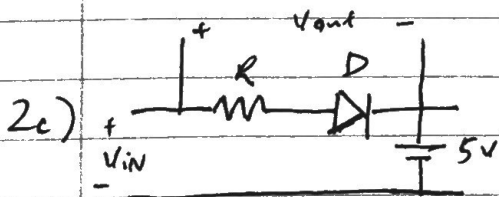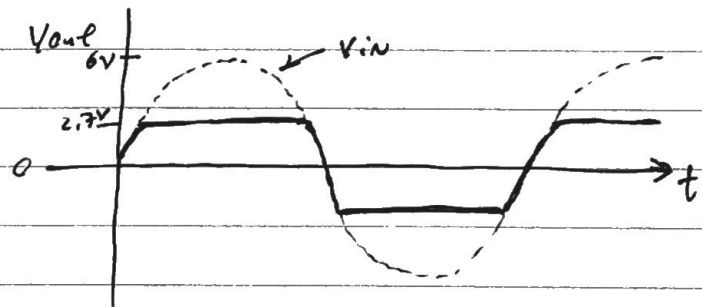

V_out always just $V_{in} - 5V$

input/output characteristic:

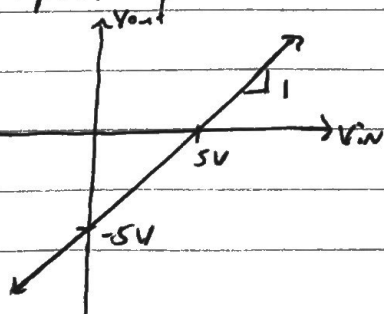

V_out vs. time:

