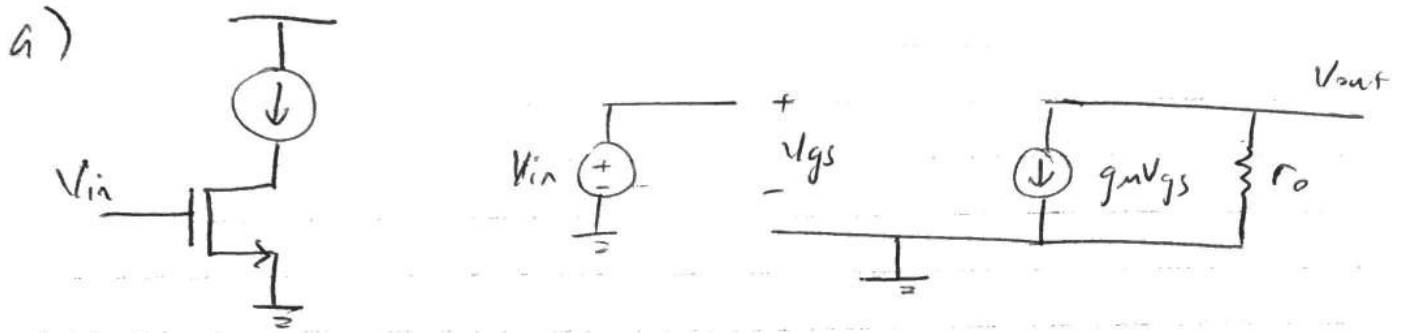


Common-source stage. w/ current source load




$$V_{out} = -g_m V_{gs} r_o = -g_m V_{in} r_o$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -g_m r_o$$

$$R_{out} = r_o \quad (\text{since } V_{gs} = 0, \text{ no current flows through the VCCS})$$
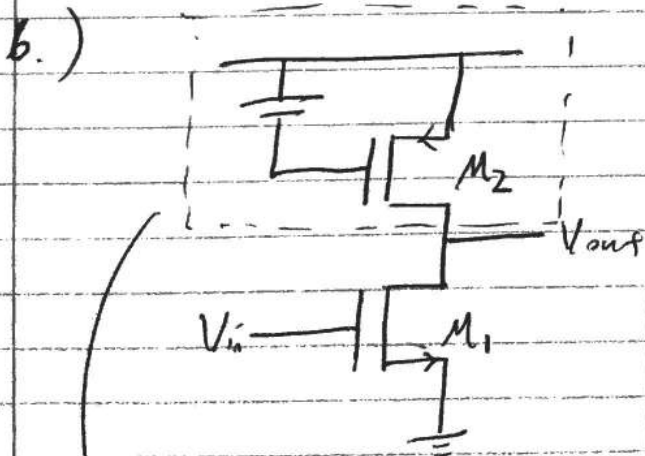
$$\begin{aligned} A_v &= -g_m r_o \\ R_{out} &= r_o \\ R_{in} &= \infty \end{aligned}$$



$$\begin{aligned} A_v &= -g_{m1} (r_{out1} \parallel r_{out2}) \\ &= -g_{m1} (r_{o1} \parallel r_{o2}) \\ R_{out} &= r_{out1} \parallel r_{out2} = r_{o1} \parallel r_{o2} \\ R_{in} &= \infty \end{aligned}$$


↓ find impedance looking into the drain (R_{out2})

by the symmetry of NMOS and PMOS, impedance looking into the drain $R_{out2} = r_{o2}$

A diode-connected device.



or

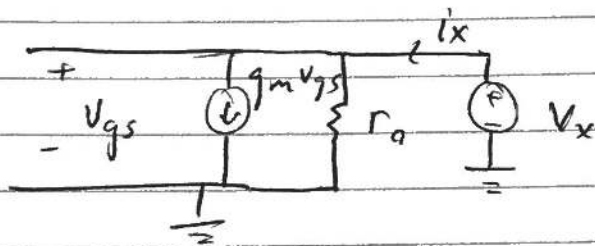

~~$i_x = g_m v_x + \frac{v_x}{r_o}$~~


$$i_x = g_m v_x + \frac{v_x}{r_o}$$

$$i_x = v_x \left(g_m + \frac{1}{r_o} \right)$$


$$R_{out} = \frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{r_o}} \cdot \frac{\frac{r_o}{g_m}}{\frac{r_o}{g_m}} = \frac{r_o \cdot \frac{1}{g_m}}{r_o + \frac{1}{g_m}} = \left(r_o \parallel \frac{1}{g_m} \right)$$

$$R_{out} = r_o \parallel \frac{1}{g_m}$$

CS stage w/ Diode-connected load,

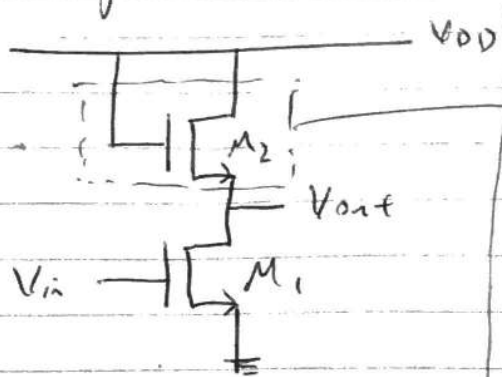

→ impedance looking into the source:

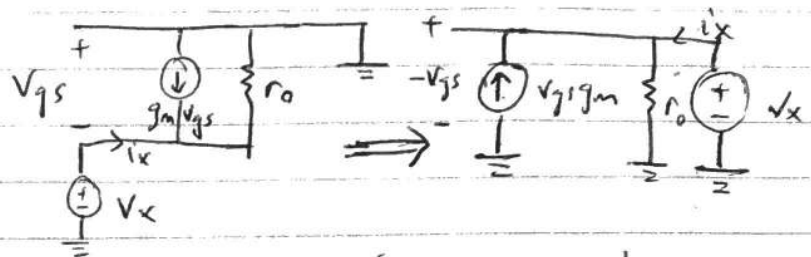

$$\frac{V_x}{i_x} = r_{o1} \parallel \frac{1}{g_{m2}} \text{ again}$$

b) assume $\lambda \neq 0$:

$$R_{out} = R_{out1} \parallel \text{Impedance looking into source of } M_2$$

$$= r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

$$A_v = -g_{m1} R_{out} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$

$$R_{in} = \infty$$

for $\lambda = 0$ case, assume $r_{o1} = r_{o2} = \infty$.

a) $\lambda = 0$

$$A_v = -\frac{g_{m1}}{g_{m2}}$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_{m2}}$$

b) $\lambda \neq 0$




$$A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}})$$

$$R_{in} = \infty$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

Common-Source w/ Degeneration.

assume $\lambda = 0$

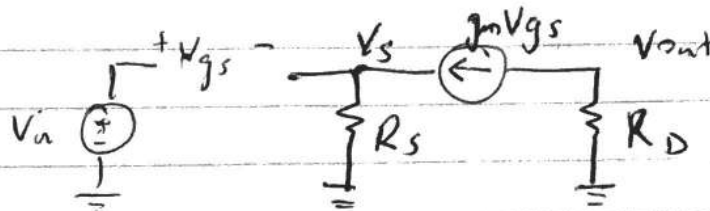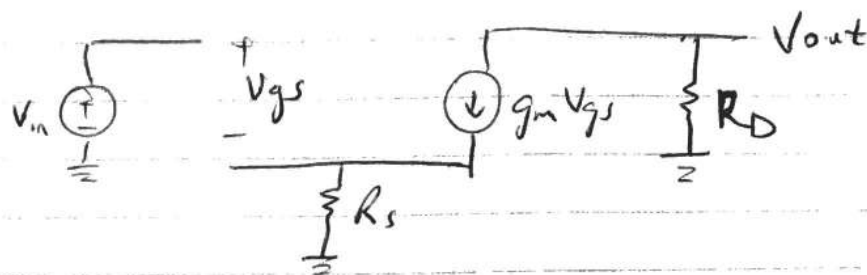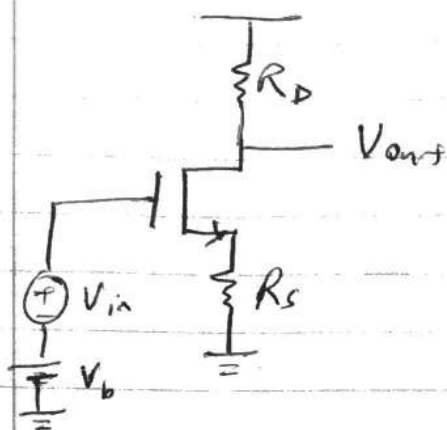

$$V_{gs} = V_{in} - V_s$$

$$g_m (V_{in} - V_s) = \frac{V_s}{R_s} = -\frac{V_{out}}{R_D}$$

$$V_s = \frac{R_s}{R_D} V_{out}$$

$$g_m \left(V_{in} + \frac{R_s}{R_D} V_{out} \right) = -\frac{V_{out}}{R_D}$$


$$V_{in} (g_m R_D) = -V_{out} (1 + g_m R_s)$$


$$\frac{V_{out}}{V_{in}} = -\frac{g_m R_D}{1 + g_m R_s}$$

$$= -\frac{R_D}{\frac{1}{g_m} + R_s} = A_v$$

(assuming $\lambda = 0$)

R_{out} (assuming $\lambda \neq 0$).

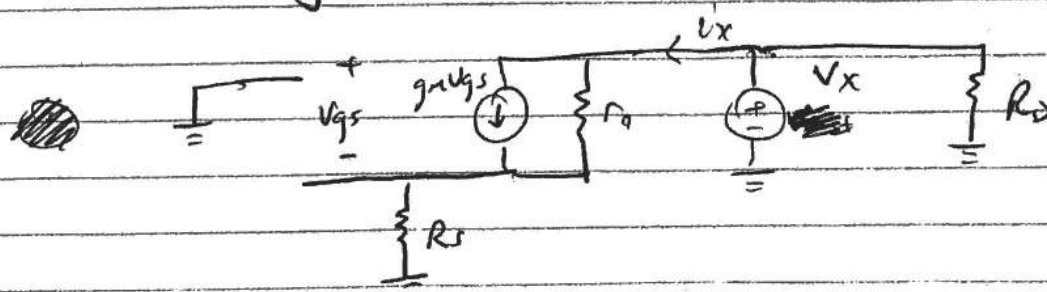

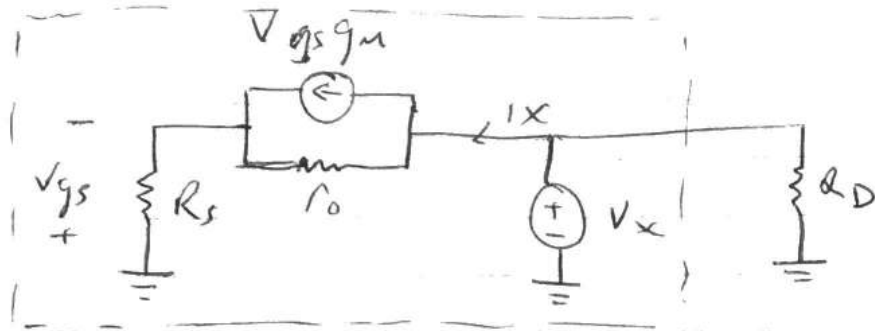

To make calcs easier ignore R_D for now


$$i_x = \frac{-V_{gs}}{R_s} = g_m V_{gs} + \frac{V_x + V_{gs}}{r_o}$$

$$\Rightarrow V_{gs} = -i_x R_s$$

$$i_x = g_m(-i_x R_s) + \frac{V_x}{r_o} + \frac{-i_x R_s}{r_o}$$

$$i_x \left(1 + g_m R_s + \frac{R_s}{r_o} \right) = V_x \left(\frac{1}{r_o} \right)$$
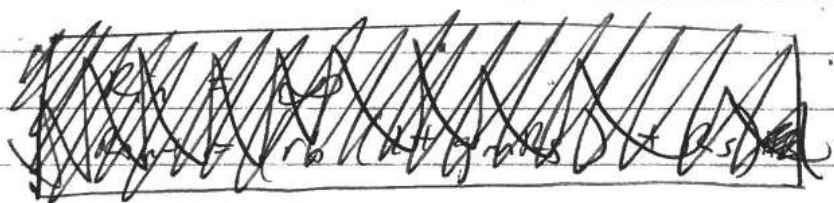
$$R_{out} = \frac{V_x}{i_x} = r_o \left(1 + g_m R_s + \frac{R_s}{r_o} \right) = r_o (1 + g_m R_s) + R_s$$




Note that this is in parallel with R_D

So: $R_{in} = \infty$

$$R_{out} = (r_o (1 + g_m R_s) + R_s) \parallel R_D$$

Example.

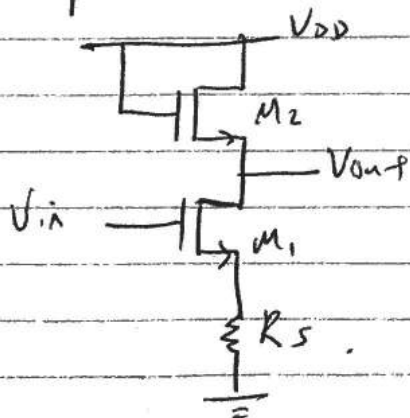

$$R_D = r_{o2} \parallel \frac{1}{g_{m2}}$$

$$R_{out} = (r_{o1} (1 + g_{m1} R_s) + R_s) \parallel (r_{o2} \parallel \frac{1}{g_{m2}})$$

assume $\lambda = 0 \Rightarrow r_{o1} = r_{o2} = \infty$


$$R_D = \frac{1}{g_{m2}}$$

$$R_{out} = \infty \parallel \infty \parallel \frac{1}{g_{m2}} = \frac{1}{g_{m2}}$$



$$A_v = -\frac{R_D}{\frac{1}{g_{m1}} + R_s} = -\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_s}$$

assuming $\lambda = 0$, $R_{out} = \frac{1}{g_{m2}}$, $A_v = -\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_s}$

Common-Gate Topology

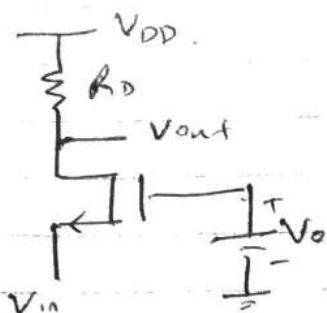


Find A_v , assume $\lambda = 0$.

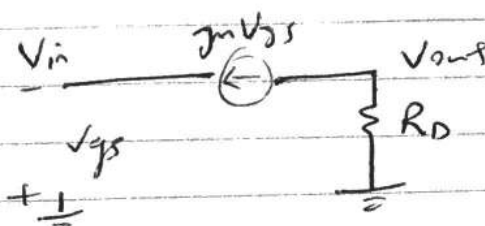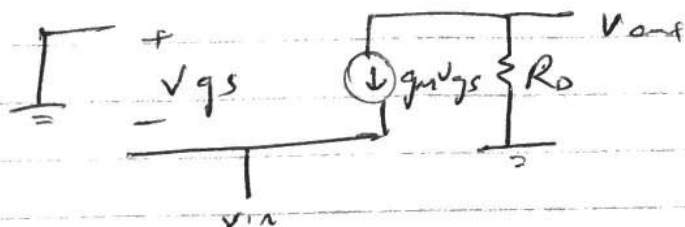


$$V_{out} = -g_m V_{gs} R_D = g_m V_{in} R_D$$
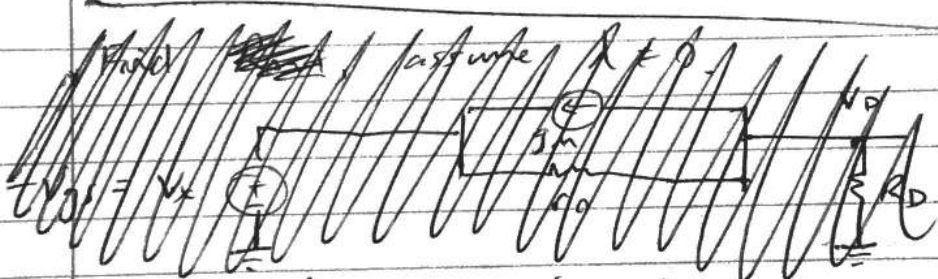
$$\Rightarrow \frac{V_{out}}{V_{in}} = g_m R_D = A_v$$



Find R_{in} , assume $\lambda = 0$.

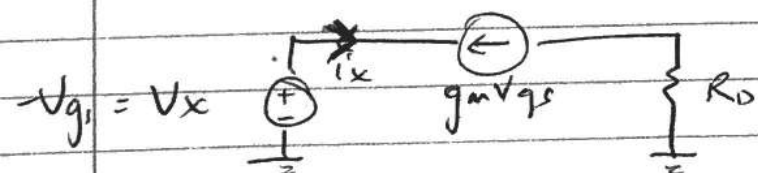


$$i_x = -g_m V_{gs}$$

$$= g_m V_x$$


$$\Rightarrow \frac{V_x}{i_x} = \frac{1}{g_m} = R_{in}$$

Find R_{out} , assume $\lambda \neq 0$.

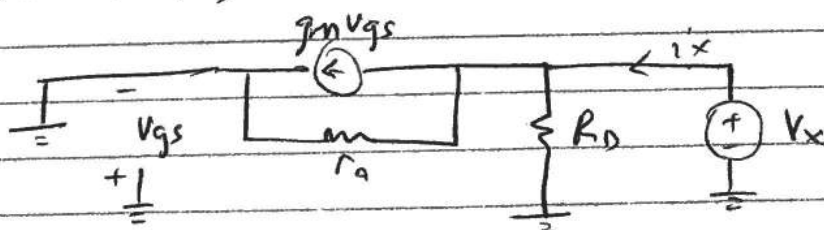

$$V_g = V_s = 0 \Rightarrow V_{gs} = 0 \Rightarrow g_m V_{gs} = 0 \Rightarrow$$
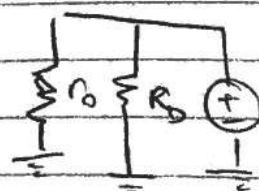
$$\Rightarrow R_{out} = R_D \parallel r_o$$



$$\text{if } \lambda = 0, r_o = \infty, R_{out} = R_D$$

Common Gate Topology

$$\lambda = 0$$

$$A_v = g_m R_D$$


$$R_{out} = R_D$$

$$R_{in} = \frac{1}{g_m}$$

$$\lambda \neq 0$$

$$R_{out} = r_o \parallel R_D$$

Cascade Example

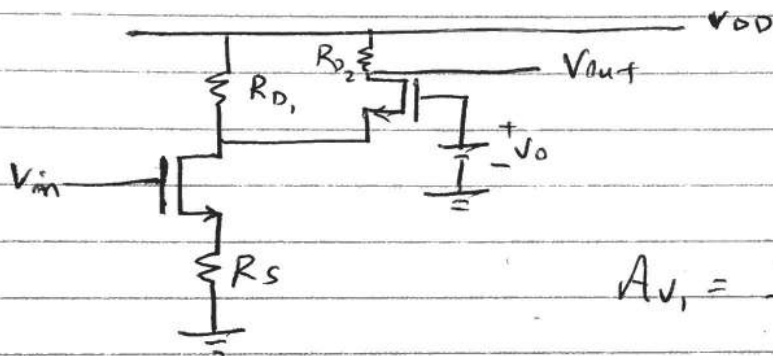

$$\lambda = 0$$

$$A_v = A_{v1} A_{v2}$$

$$A_{v1} = - \frac{R_D \parallel R_{in2}}{\frac{1}{g_{m1}} + R_S}$$


$$A_{v2} = g_{m2} R_{D2}$$

$$R_{in2} = \frac{1}{g_{m2}}$$

$$A_v = - \left(\frac{R_D \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S} \right) (g_{m2} R_{D2})$$

Source Follower

$$\lambda \neq 0$$

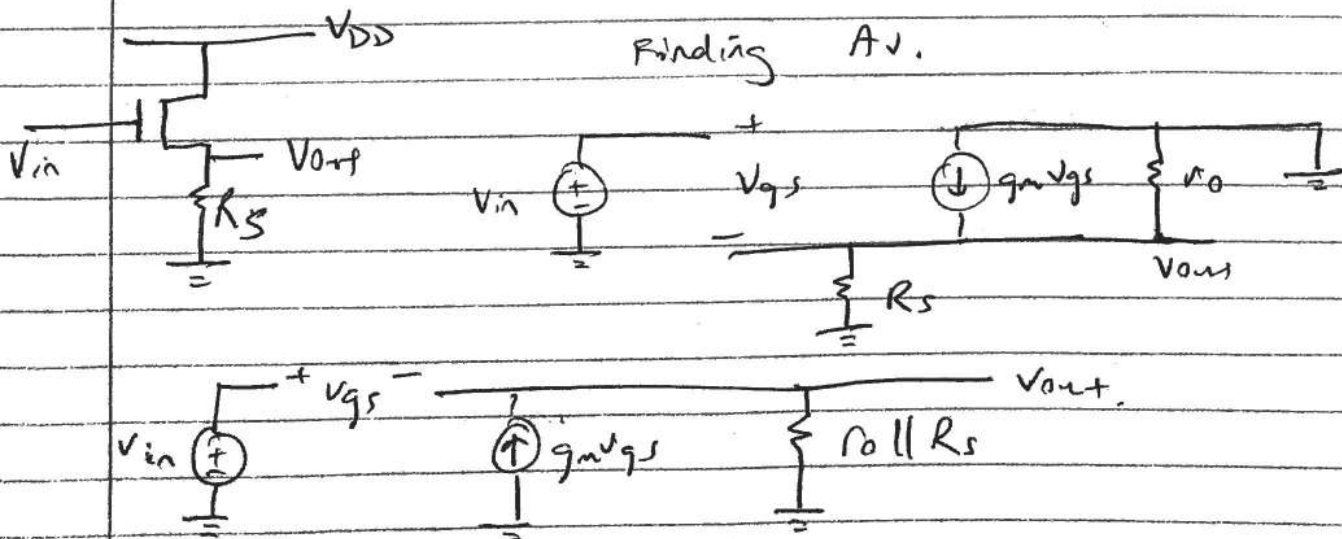


$$V_{out} = g_m V_{gs} (R_s \parallel r_o) \\ = g_m (V_{in} - V_{out}) (R_s \parallel r_o)$$

$$V_{out} (1 + g_m (R_s \parallel r_o)) = V_{in} (g_m (R_s \parallel r_o))$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m (R_s \parallel r_o)}{1 + g_m (R_s \parallel r_o)} = \frac{R_s \parallel r_o}{\frac{1}{g_m} + (R_s \parallel r_o)}$$

Finding R_{in} , $\lambda \neq 0$. $R_{in} = \infty$.

Finding R_{out} , $\lambda \neq 0$.

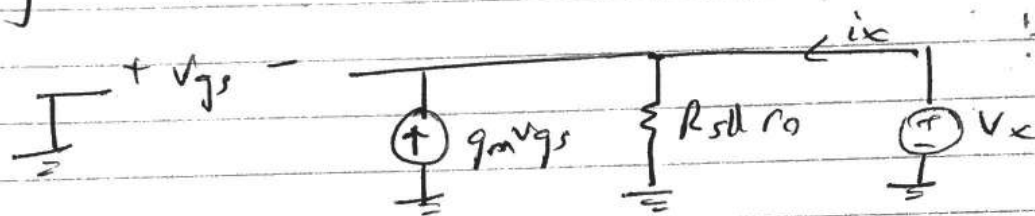

$$V_{gs} = -V_x$$

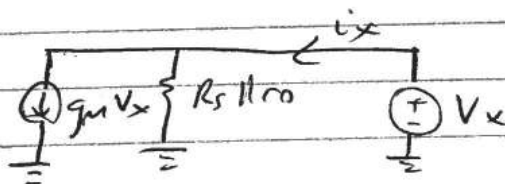

impedance of current source in parallel w/ resistance

$$R_{out} = \frac{1}{g_m} \parallel (R_s \parallel r_o)$$

Source Follower

a) $\lambda = 0$

$$A_v = \frac{R_s}{\frac{1}{g_m} + R_s}$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_m} \parallel R_s$$


b) $\lambda \neq 0$.

$$A_v = \frac{R_s \parallel r_o}{\frac{1}{g_m} + R_s \parallel r_o}$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_m} \parallel R_s \parallel r_o$$

Cascade Example.

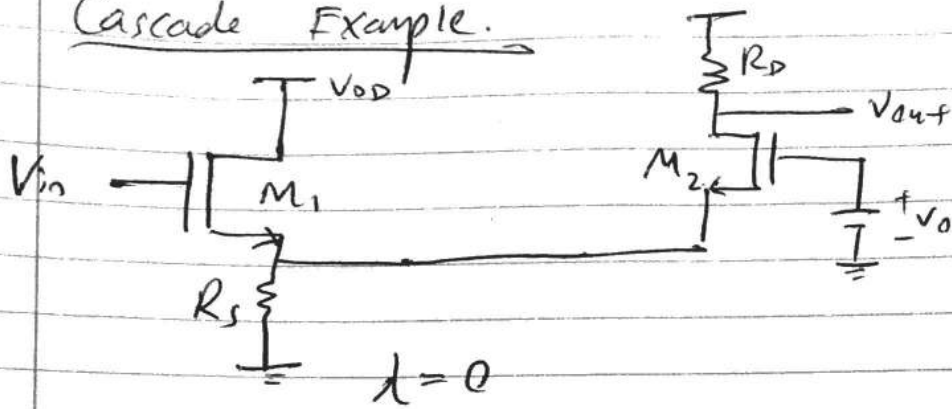

$$A_v = A_{v1} A_{v2}$$

$$A_{v1} = \cancel{\text{value}} \cdot \frac{R_S \parallel R_{in2}}{\frac{1}{g_{m1}} + R_S \parallel R_{in2}}$$

$$R_{in2} = \frac{1}{g_{m2}}$$

$$A_{v2} = g_{m2} R_D$$

$$A_v = \left(\frac{R_S \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S \parallel \frac{1}{g_{m2}}} \right) (g_{m2} R_D)$$